



UNIVERSITY OF TEHRAN

Electrical and Computer Engineering Department

Digital Logic Design, ECE 367, Digital System I, 894, Fall 1403

Computer Assignment 5&6


RTL Accelerator Design

Name:	Username:
Date:	Student Number:

In this assignment, you are to design a Restoring divider accelerator and interface it with an 8-bit bus for burst mode operation.

 Part 1: Divider Module Design

You are to design a Sequential Divider accelerator that uses the Restoring divide algorithm. The divider takes two 16-bit inputs, Dividend (A) and Divisor (B). After receiving the *start* positive pulse, the module captures the inputs at the rising edge of the clock. This input capturing should occur in a single clock cycle. After performing the division algorithm on the received inputs, the module gives two 16-bit outputs that are Remainder (R) and Quotient (Q) and issues a *ready* signal. This signal remains active until the next division operation begins. Note that the inputs are being captured in burst mode.




- Show the complete Data path and controller of your design.
- Write the Verilog description of the module.

- c) Simulate the module with different test cases such as Positive dividend and divisor, Negative dividend and divisor, Zero divisor (ensure proper error handling),...

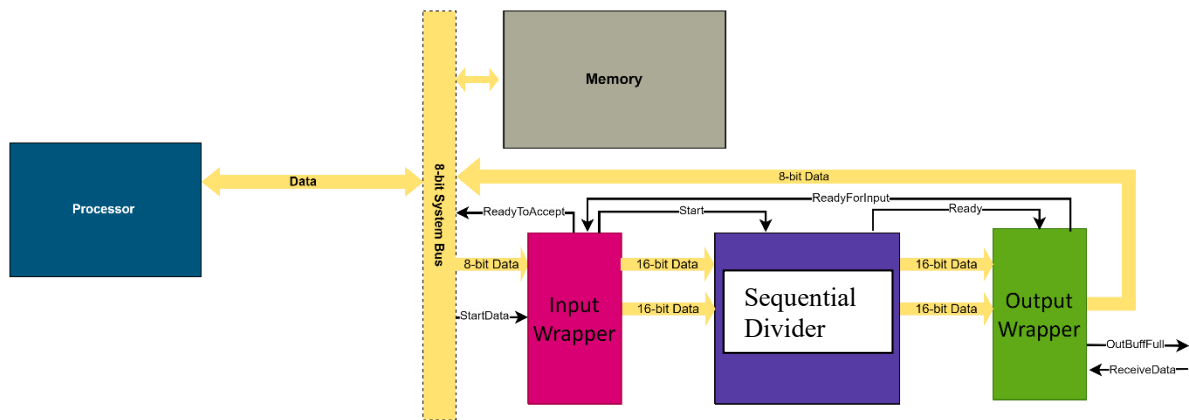Part 2: 8-Bit Bus Interfacing

Your Divider will function as an accelerator in a system with an 8-bit data bus as shown below:



- Design an input wrapper to accept burst inputs from an 8-bit bus for the dividend and divisor. The wrapper issues a *ReadyToAccept* signal to indicate that it is ready to receive data. After receiving a *StartData* positive pulse, the inputs are buffered internally. Once the *ReadyForInput* signal is asserted, the 16-bit data is provided to the Divider module as its operands, and the *start* signal is asserted for the Divider.
- Design an output wrapper to collect 16-bit results (Quotient and Remainder) from the Divider module and send them in burst mode over an 8-bit bus. The output wrapper begins data transfer after receiving the *Ready* signal from the Divider. It then asserts the *OutBuffFull* signal to indicate that data is ready for transfer. Upon receiving the *ReceivedData* signal from the bus controller, it starts the data transfer process. Once the data transfer is completed, the wrapper issues the *ReadyForInput* signal and prepares to receive the next set of data.
- Write the Verilog description of the input, output wrappers and connect them to your divider and test the whole design. Show your results.

Deliverables:

Generate a report that includes all the items below:

- For Part 1 show your Data path and Controller diagram on paper.
- For other parts, show simulation results. Your simulation run and the project built for this purpose must be demonstrated to the TA.
- For all parts, project files, and results must be demonstrated to the TA. Using waveforms, circuit diagrams, and other circuit representations justify your answers.

Make a PDF file of your report and name it with the format shown below:

FirstinitialLastnameStudentnumber-CA nn -ECE mmm

Where *nn* is a two-digit number for the Computer Assignment, *mmm* is the three-digit course number under which you are registered, and hopefully you know the rest. For the *Firstinitial* use only one character. For *Lastname* and for the multi-part last names use the part you are most identified with. Use the last five digits of your student id (exclude 8101) for the *Studentnumber* field of the report file name.